

Chapter 4

The Processor

[Some slides adapted from A. Sprintson, M. Irwin, D. Paterson and others]

Reading Registers “Just in Case”


- Note that both RegFile read ports are active for all instructions during the Decode cycle using the *rn* and *rm* instruction field addresses
 - Since haven't decoded the instruction yet, *we don't know what the instruction is!*
 - Just in case the instruction uses values from the RegFile do “work ahead” by reading the two source operands

Which instructions do make use of the RegFile values?

- Also, all instructions (except **B**) use the ALU after reading the registers


Fetching Instructions

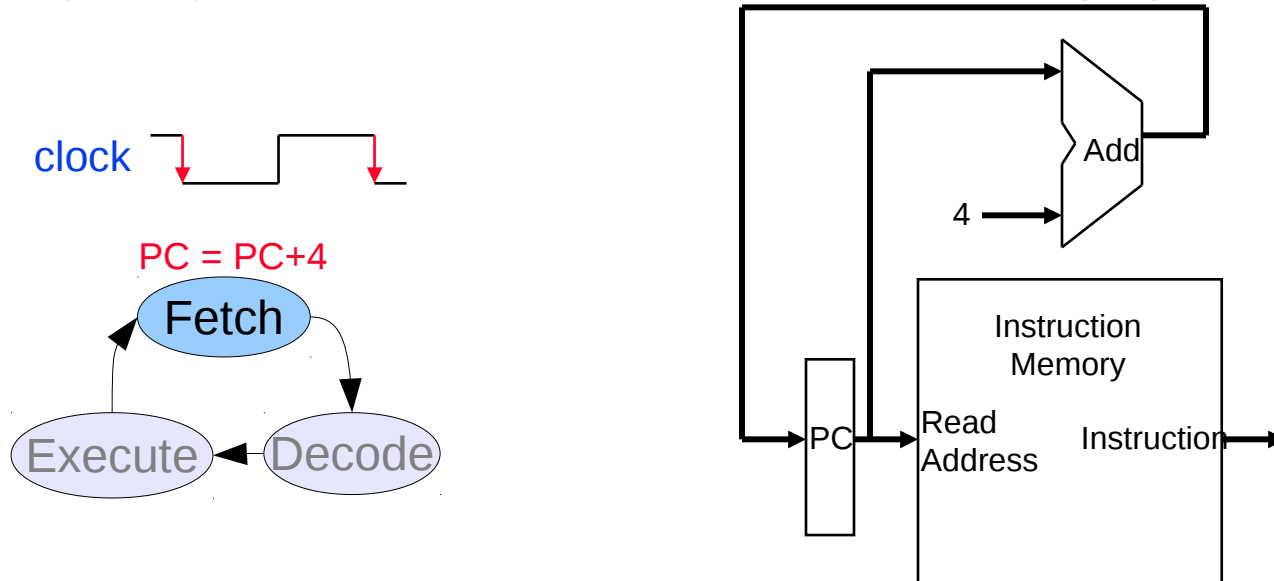- Fetching instructions involves
 - reading the instruction from the Instruction Memory
 - updating the PC value to be the address of the next (sequential) instruction




- PC is updated every clock cycle, so it does not need an explicit write control signal
- Instruction Memory is read every clock cycle, so it doesn't need an explicit read control signal

Instruction Fetch

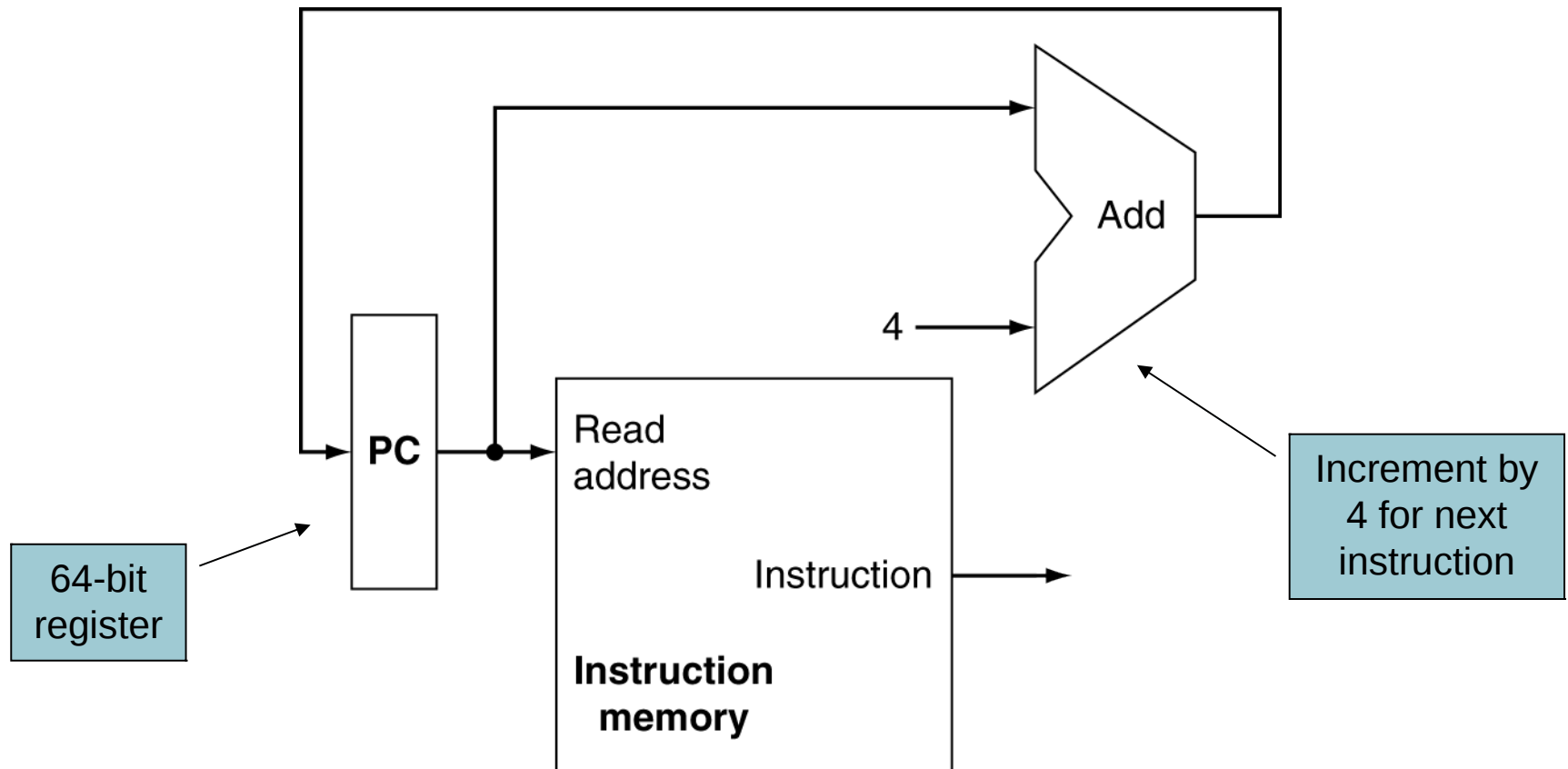


Decoding Instructions

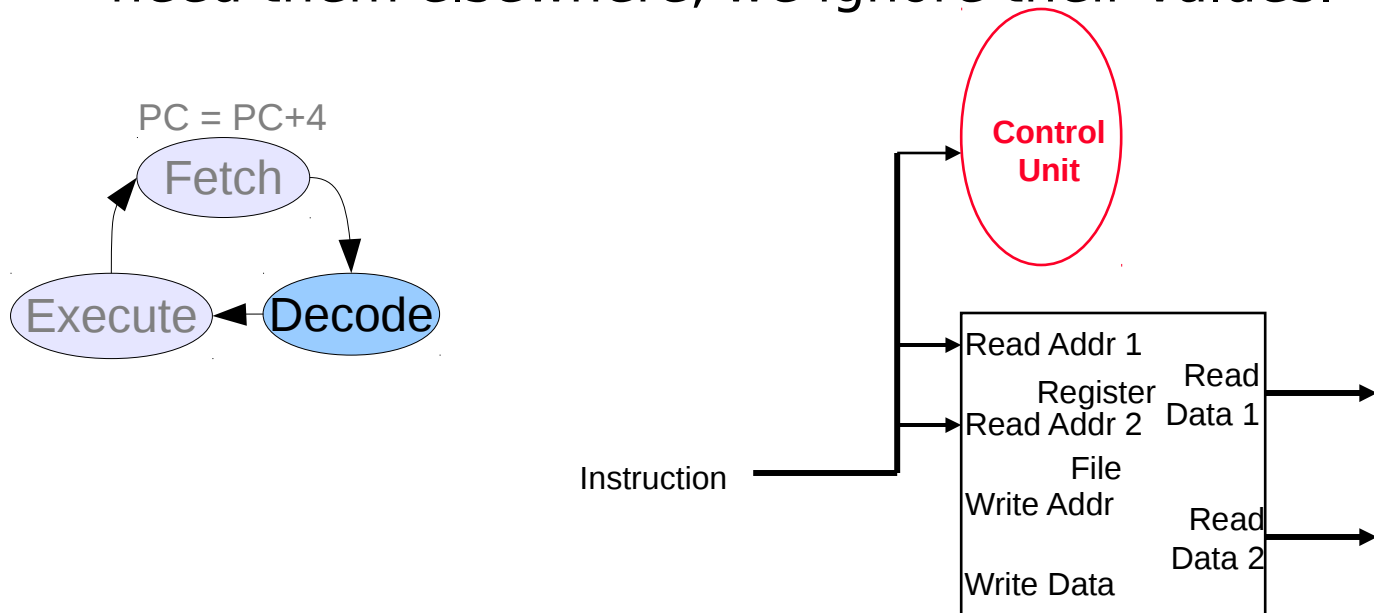- Send the fetched instruction's opcode to the control unit
- Read two values from the Register File
 - Register File indices are contained in the instruction
 - Read data outputs are always enabled. If we don't need them elsewhere, we ignore their values.




R-Format Instructions

 - Read two register operands
- Perform arithmetic operation
- Write register result



R-Format Instructions

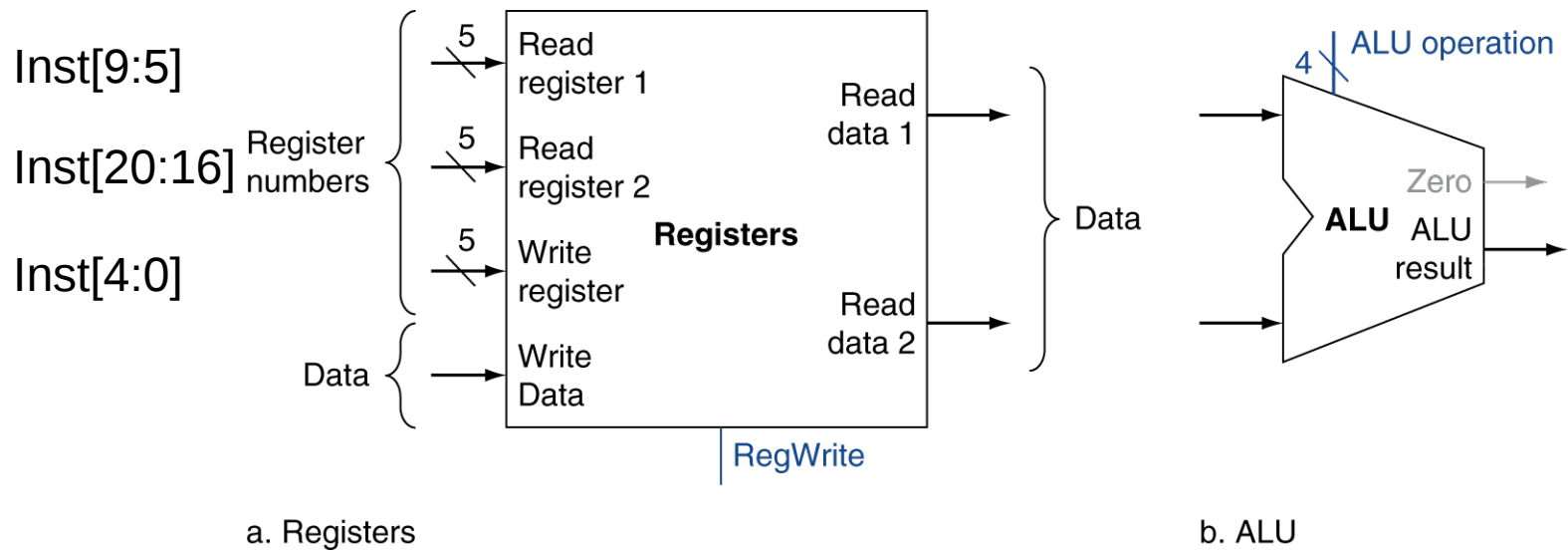- Read two register operands
- Perform arithmetic operation
- Write register result




Load/Store Instructions

- Read register operands
- Calculate address using up to 9-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory




Load/Store Instructions

 
- Read register operands
- Calculate address using up to 9-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



a. Data memory unit

 

b. Immediate Generator Unit

 


b. ALU

Branch Instructions

- Read register operand
- Test for zero
 - Use ALU, check Zero output
- Calculate target address
 - Sign-extend immediate
 - Shift left 2
 - Add to PC





Branch Instructions

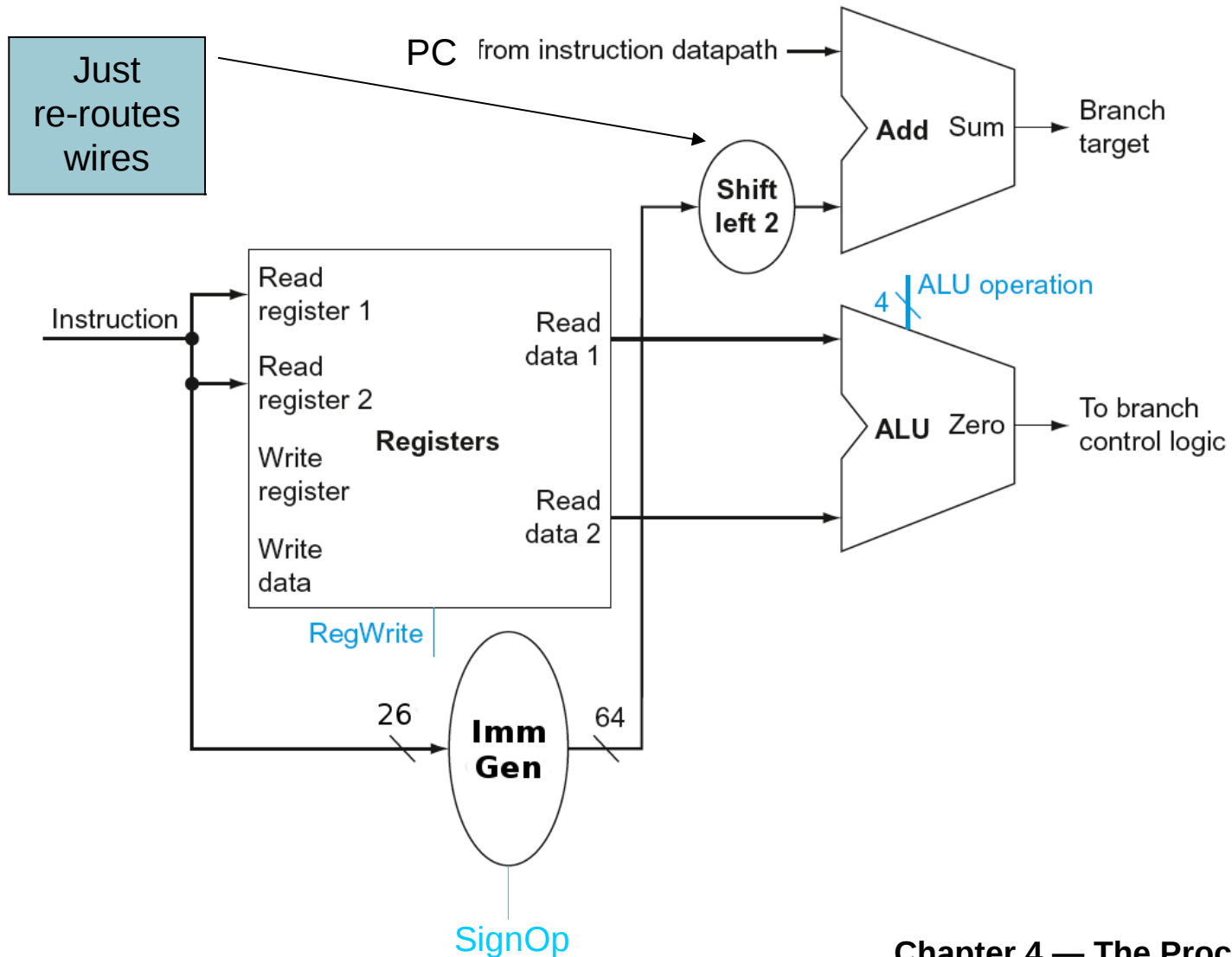



Composing the Elements

- First-cut data path does an instruction in one clock cycle
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions


Constructing a single Datapath:R-type

  

  Constructing a single Datapath: R-type, D-Type



R-Type/Load/Store Datapath

 

Full Datapath: Adding B-Type

